
2025 Digital IC Design Homework 2

NAME	簡紹軒	ur ie Design ii		
Student ID	P76131474			
Functional Simulation Result				
Pattern1	Pattern2	Pattern3	Pattern4	Pattern5
Pass	Pass	Pass	Pass	Pass
Pattern 1				
# All data have been generated successfully! #				
Pattern 2				
# All data have been generated successfully! #				
Pattern 3				
# All data have been generated successfully! #				
<pre># # ** Note: \$finish : C:/Users/P76131474/Desktop/DIC_HW/HW2_LCD_Controller/file/testfixture.sv(171) # Time: 1615 ns Iteration: 0 Instance: /testfixture</pre>				
Pattern 4				
<pre># All data have been generated successfully! #</pre>				

LCD CTRL Finite-State Machine Design:

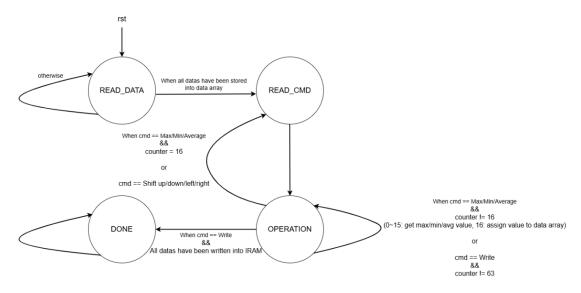

READ_DATA: 把所有在 IROM 裡面的資料全部讀進宣告的 data array 裡面,讀完後會進入下一個 state。

READ_CMD: 讀取 cmd, 1 clock 之後進入下一個 state。

OPERATION: 根據 cmd 會做不同的事情。

如果 cmd 是 Shift up/down/left/right,則移動點座標後結束,回到 READ CMD state 讀取下一個指令;

如果 cmd 是 Max/Min/Average,則會先找到最大/最小/平均值,再將找到的值存進 data array 裡面後結束,回到 READ CMD state 讀取下一個指令;

如果 cmd 是 Write,則會把 data array 裡面的所有資料寫進 IRAM 後結束,進入 DONE state。

DONE:把 done 訊號設為 1。